

# LABORATORY 1 : Gate Design

---

VLSI .Curs 20-21. Cuatrimestre de tardor

Autors: Carlos Rodriguez  
Victor Correal

Professor : Ramon Canal

Data : 02/10/2020


# LAB 1: Gate Design

## 1. Work Time

8h between understanding the program and working in the laboratory

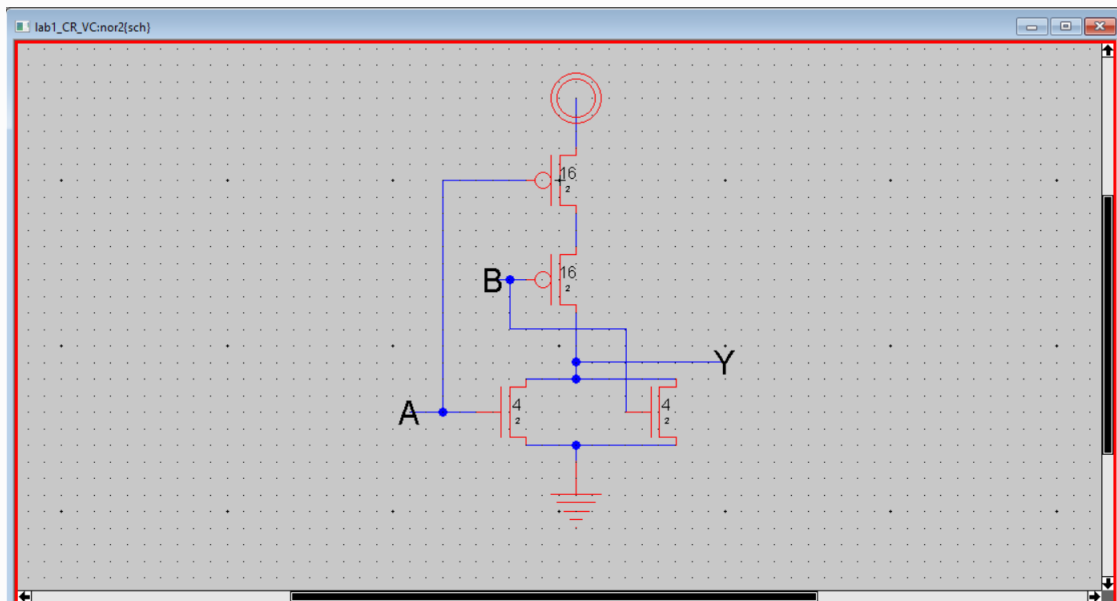
## 2. Schematic nor2

Schematic consisting of 2 transistors pMOS in series and 2 transistors nMOS in parallel. NOR with 2 inputs and 1 output



 
### 2.1 Waveform simulate nor2

We see that for the values  $A=0$  and  $B=0$ ,  $Y=1$




### 3. Layout nor2

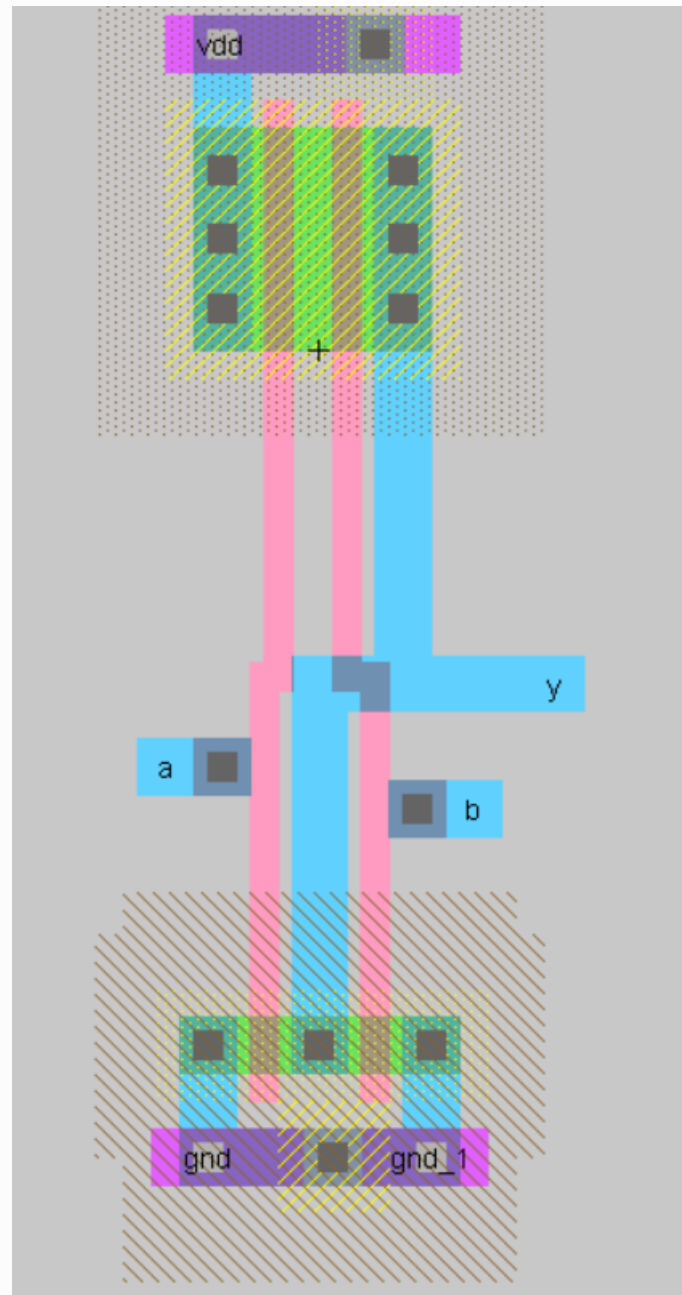

## 2.1 Layout Verification Nor2


### 2.1.1 DRC

PASS!

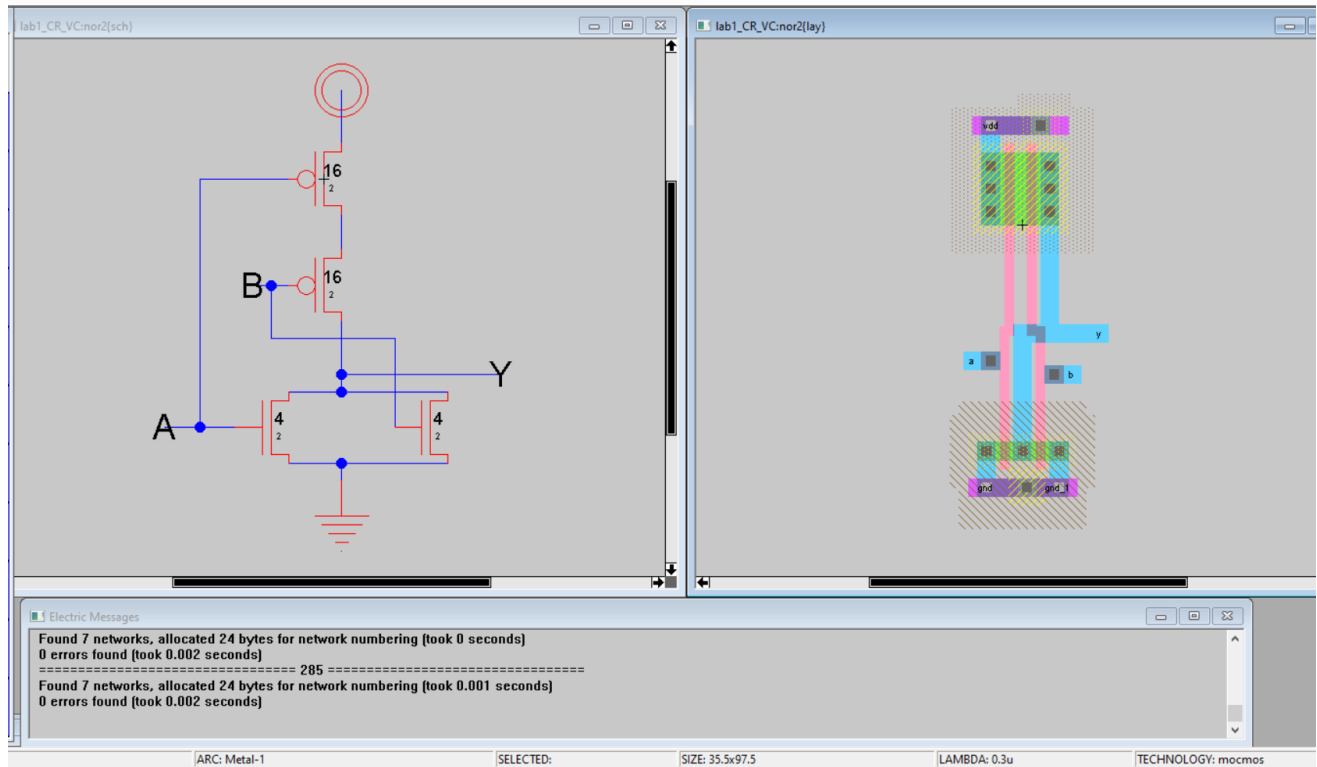


### 2.1.2 ERC

PASS!

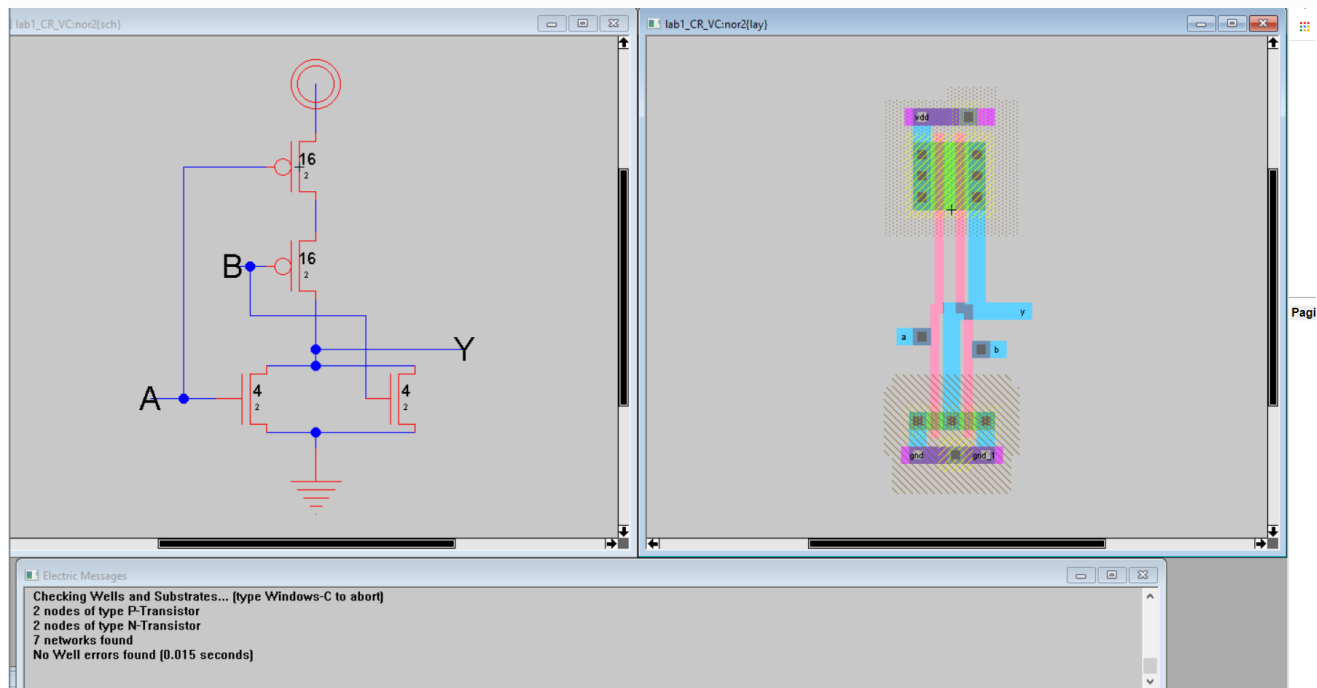


## 2.1.3 NCC

PASS!

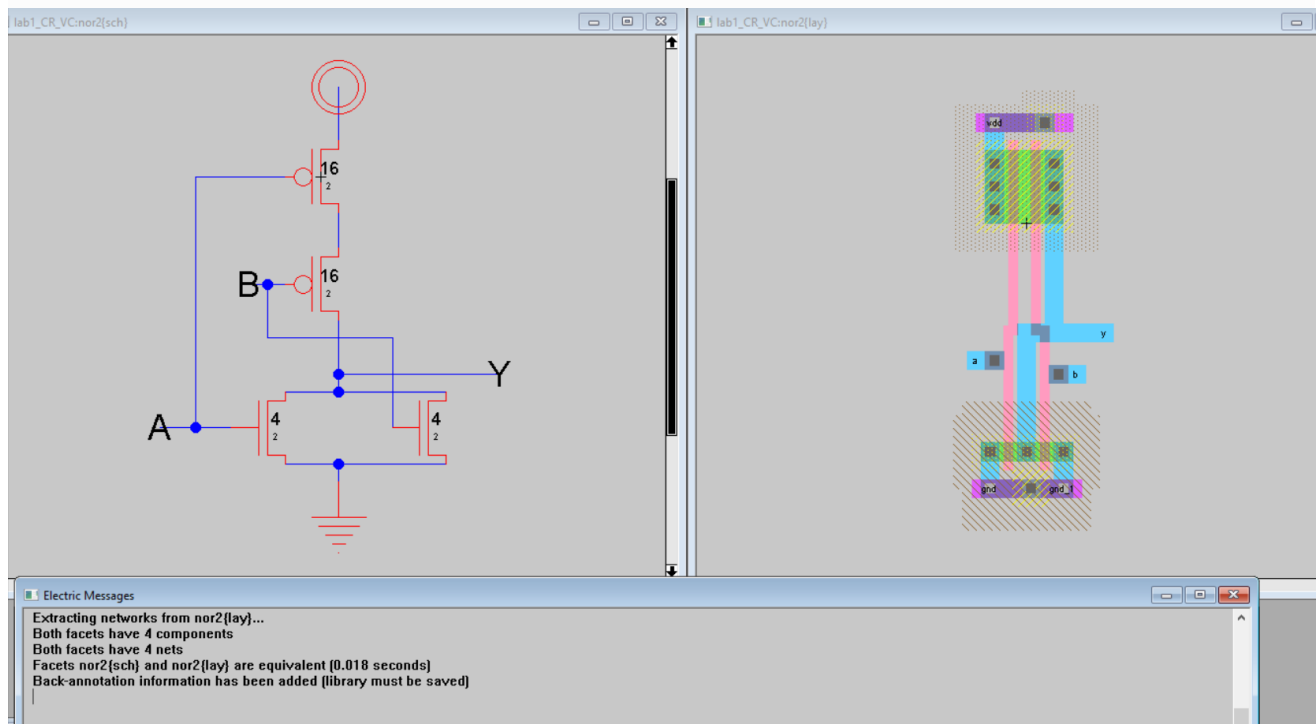

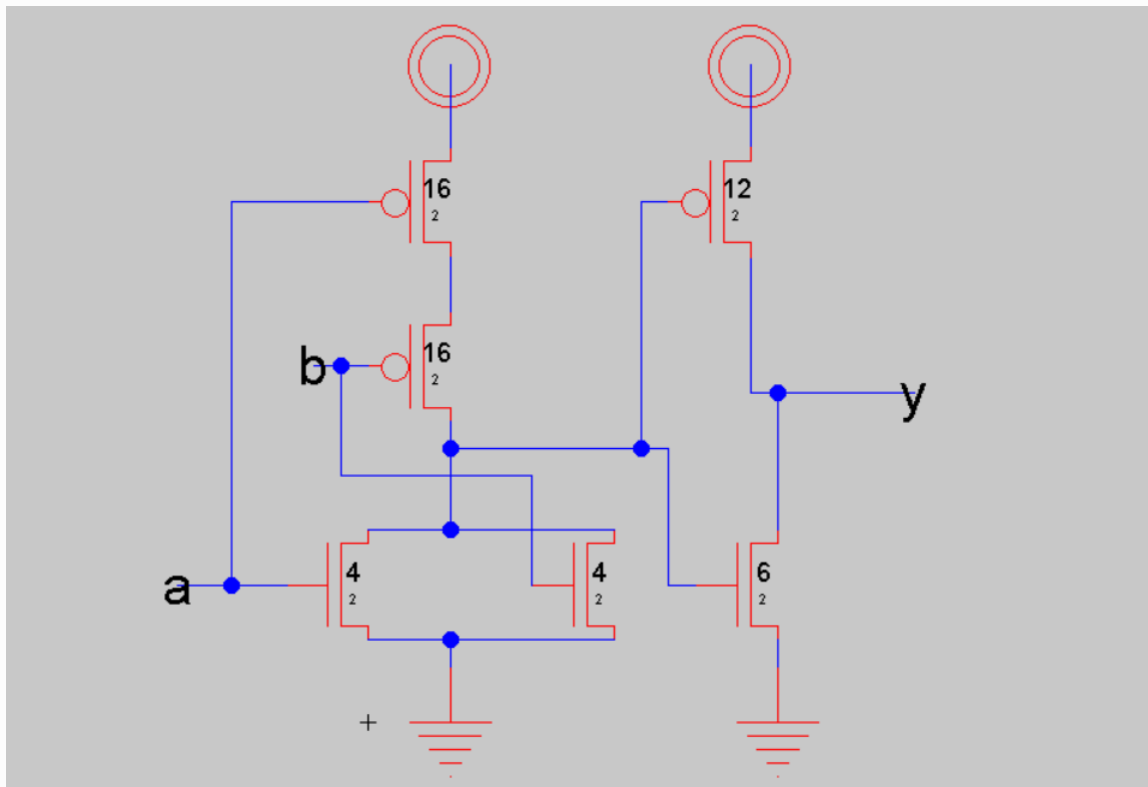
## 4. Schematic Or2


Schematic consisting in one 2-NOR and 1-INV. OR with 2 inputs and 1 output



## 5. Layout Or2

 


### 5.1 Icon Or2

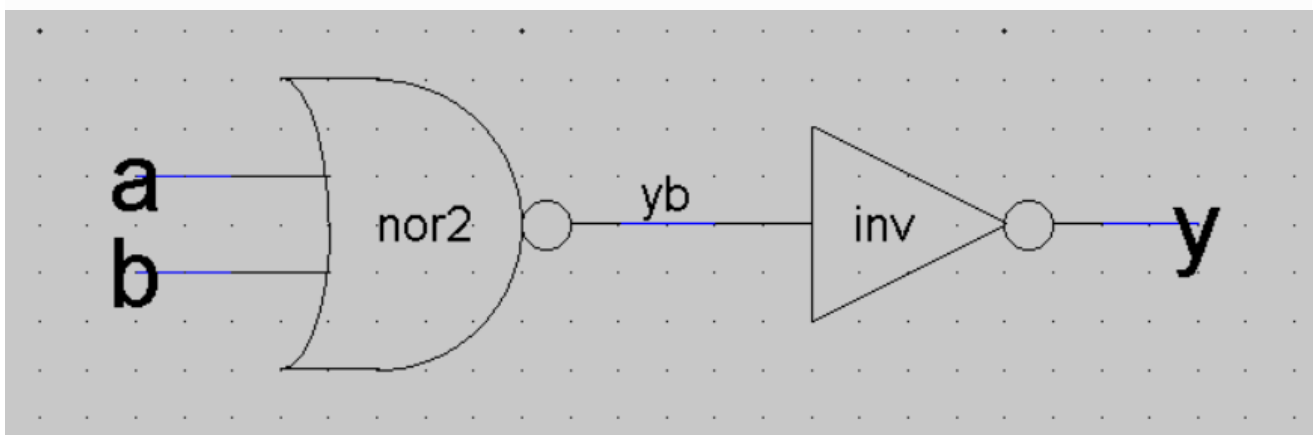
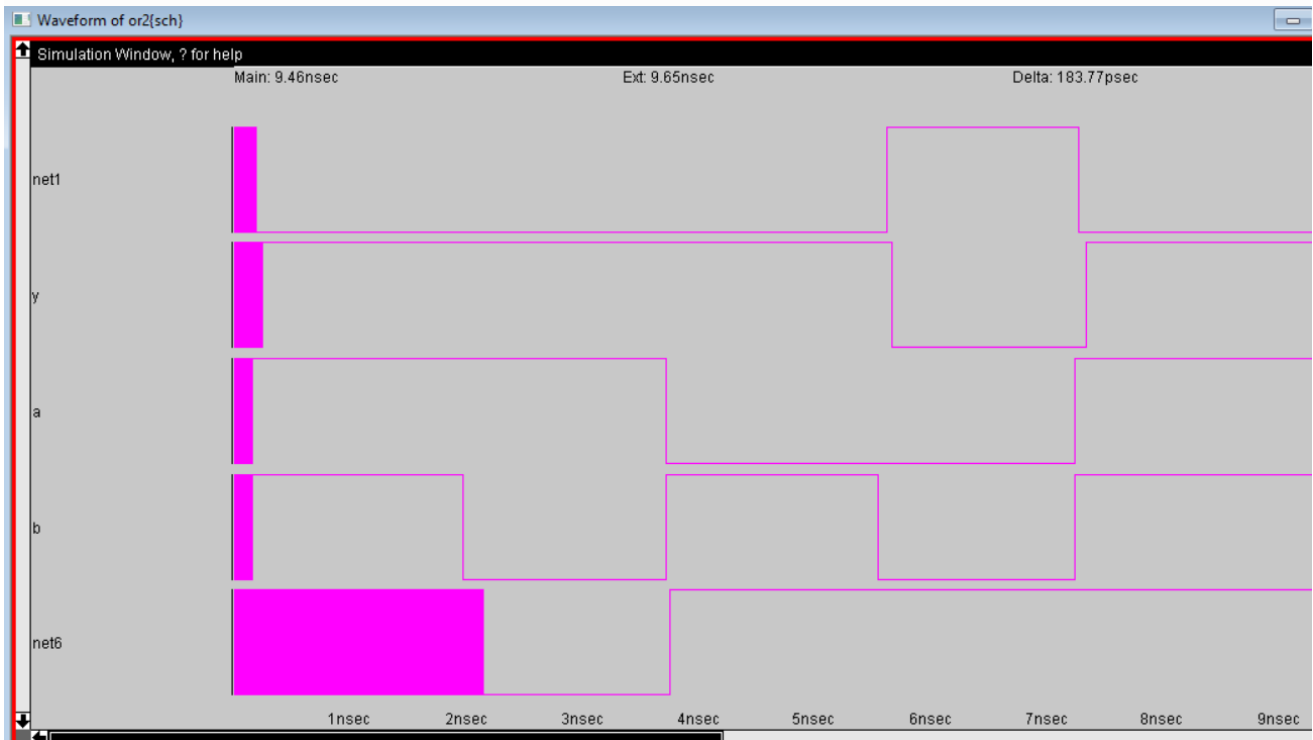
## 6. Waveform simulate Or2


We see that for the values  $A=1$  or  $B=1$ ,  $Y=1$




## 7. Layout Verification Or2

We see in the image the result of verification

### 7.1 DRC

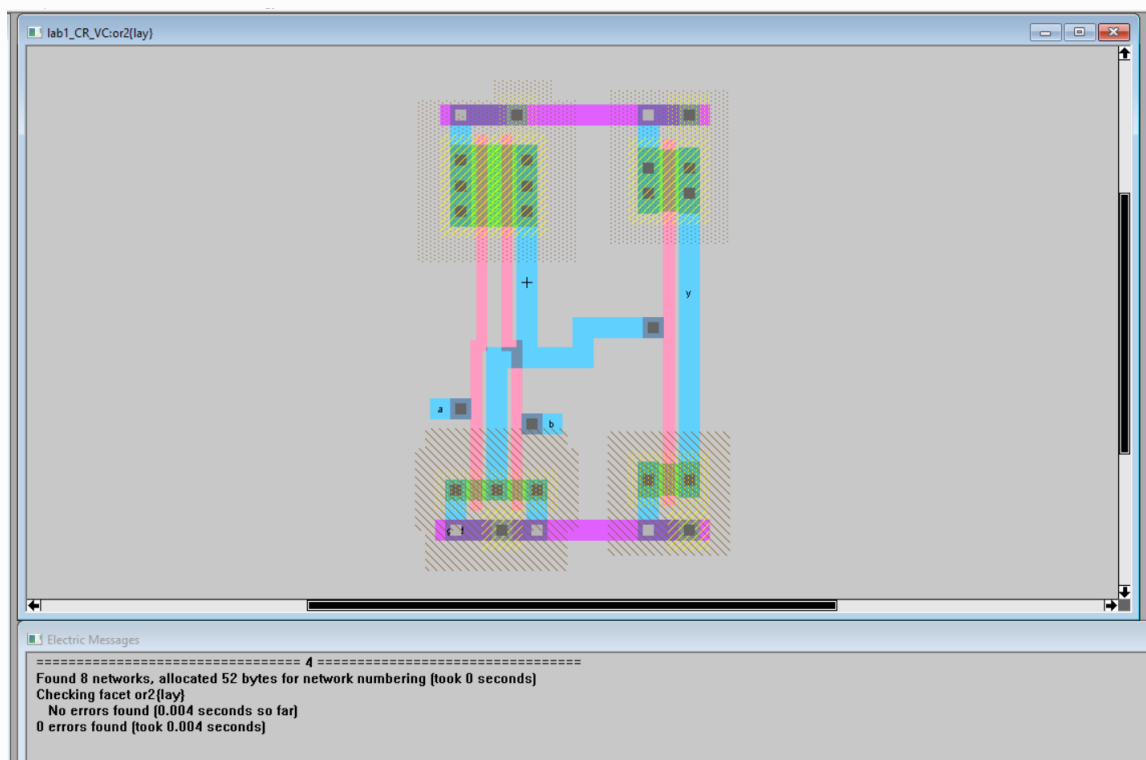

## 7.2 ERC

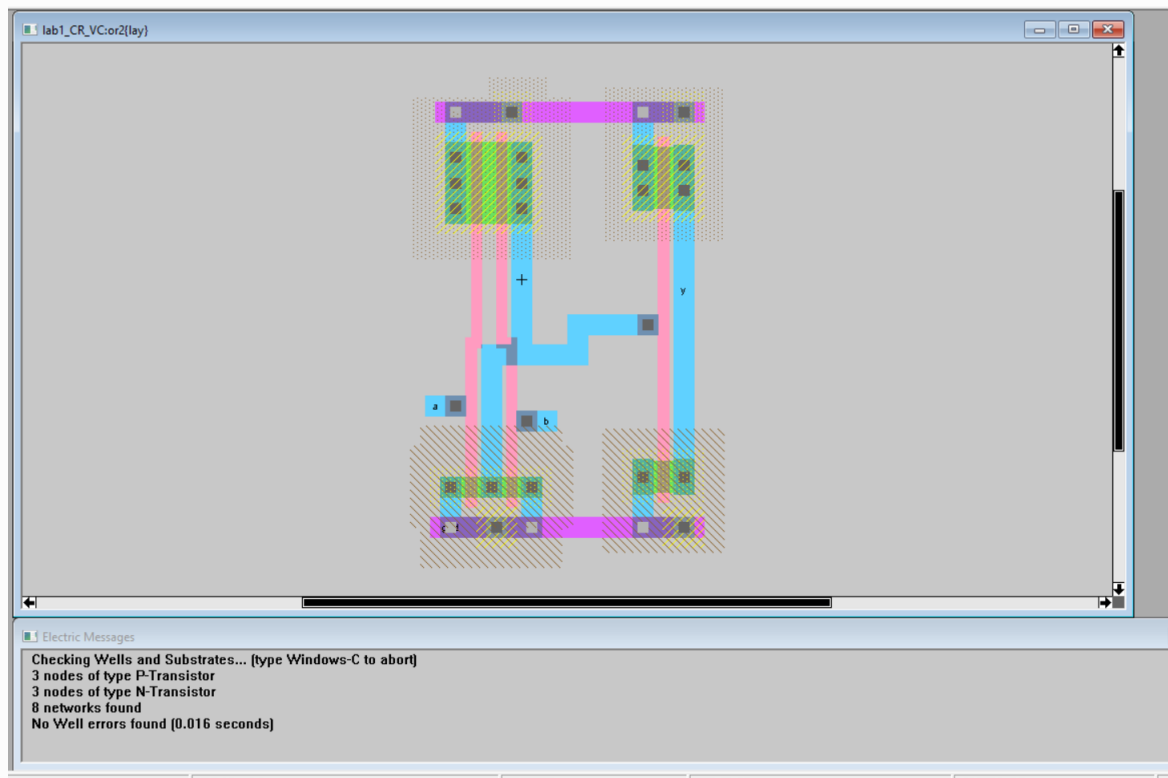

## 7.3 NCC

